 


DIGITAL ELECTRONICS


Lecture Note 02: Boolean Algebra and Logic Gates



Dr. Tushar Kanti Bera


Department of Electrical Engineering
National Institute of Technology Durgapur (NITD)
Mahatma Gandhi Rd, A-Zone, Durgapur, West Bengal 713209, India
Date: Jan-Jun, 2019

Introduction to Logic Gates

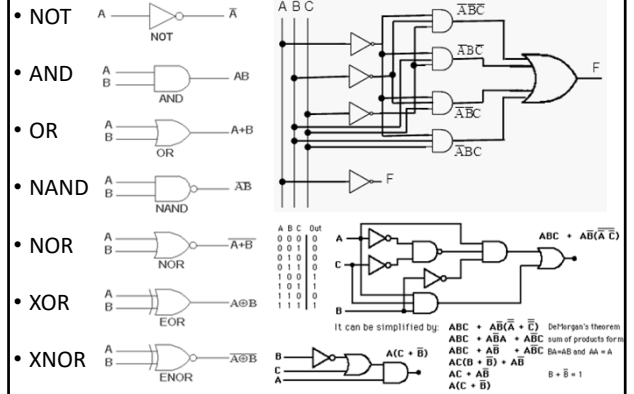

NOT Gate

 - NOT provides the inversion of the digital signal
- NOT gate is also called as Inverter



- Boolean expression or Gate Equation


$$X = \bar{A}$$

- Truth Table


A	X
0	1
1	0

74LS04 NOT Gate IC

- NOT Gate

 


7404 Hex Inverters

 

AND Gate

 - AND gate provides the AND operation of the digital signal



- Boolean expression or Gate Equation



$$X = A.B$$

- Truth Table

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1


AND Gate IC

  - AND gate provides the AND operation of the digital signal



OR Gate

 - OR gate provides the OR operation of the digital signal



- Boolean expression or Gate Equation


$$X = A + B$$

- Truth Table

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1


OR Gate IC

 - OR gate provides the OR operation of the digital signal



NAND Gate

 - NAND gate provides the (AND+NOT) operation of the digital signal



- Boolean expression or Gate Equation


$$X = \overline{A \cdot B}$$

- Truth Table

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1


NAND Gate IC

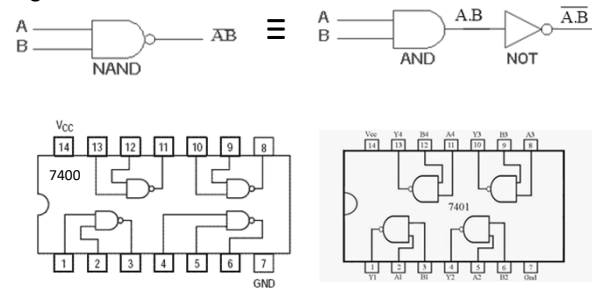- NAND gate provides the (AND+NOT) operation of the digital signal



NOR Gate

 - NOR gate provides the (OR+ NOT) operation of the digital signal



- Boolean expression or Gate Equation


$$X = \overline{A + B}$$

- Truth Table

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

XOR Gate

 
- XOR gate provides the exclusive OR operation of the digital signal



A	B	X
0	0	0
0	1	1
1	0	1
1	1	0


XNOR Gate IC

 - XNOR gate provides the exclusive NOR operation of the digital signal





$$X = A.B + \bar{A}.\bar{B}$$



A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

 

Gate IC Pin Diagram

  


7427

  

Gate IC Pin Diagram

 Pinout diagram of the 74HC266N, 74LS266 and CD4077 quad XNOR plastic dual in-line package 14-pin package (PDIP-14) ICs.



<http://www.wikiwand.com/en/XNOR>

<http://hyperphysics.phy-astr.gsu.edu/hbase/Electronic/xor.html>

Timing Diagram

- Timing diagram of the AND gate:

AND Gate Timing Diagram


 


Figure 3-10 Example of pulsed AND gate operation with a timing diagram showing input and output relationships.

10


Timing Diagram

- Timing diagram of the AND gate:

 


Timing Diagram

 - Timing diagram of the gates:
- Timing diagram of the digital signal is the representation of the signal amplitude with respect to time.
- The figure below shows a timing diagram of three digital signals A, B and C




Timing Diagram

 - Timing diagram of a two-input AND gate:




Timing Diagram: AND Gate

 - Timing diagram of a two-input AND gate:




Timing Diagram: AND Gate

 - Timing diagram of a two-input AND gate:



Timing Diagram: OR Gate


- Timing diagram of a two-input OR gate:

 

Timing Diagram: NOR Gate


- Timing diagram of a two-input NOR gate:

NOR Gate Timing Diagram

 


Timing Diagram: NAND Gate

- Timing diagram of the NAND gate:

 


Timing Diagram: NAND Gate

- Timing diagram of the NAND gate:

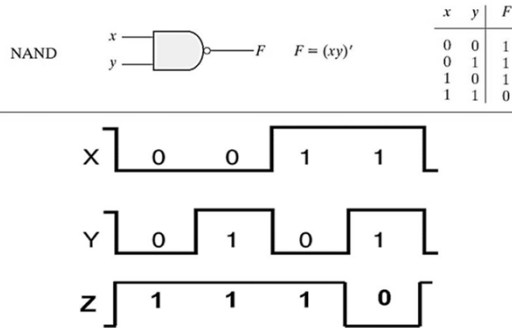


Timing Diagram: Gate Combination

 - Timing diagram of the gate combination:




Timing Diagram: XOR Gate

- Timing diagram of the XOR gate:

 


Delays in Gates and Timing Diagrams

- If the input of a logic gate is changed, the output will not change instantaneously. The reason behind this is elements that switch the inputs within the gate take a fixed time to react to change, so the resulting change output is delayed with respect to the input. The propagation delay in an inverter figure shown below any possible waveforms of input and output for an inverter. For a change in output delayed by time, ϵ , taken respectfully to the input, is said to have a propagation delay of ϵ .
- A propagation delay for a 0 to 1 output change may be different than that of a delay for a 1 to 0 change. Some propagation delays can be neglected if they are as short as a few nanoseconds. However, it is good practice to analyze these sequential circuits, no matter how short the delay may be.
- More than likely, a timing diagram will be used to analyze sequential circuits. Timing diagrams can be used to show different signals in a circuit as a function of time. When plotting numerous variables, they are plotted along the same time scale so the times at which these variables change with respect to each other can be easily understood.

 


Delays in Gates and Timing Diagrams

- For a circuit with two gates, as shown below, each gate is assumed to have propagation delay of 20 ns. The diagram specifies what will happen if gate inputs B and C are held at regular values of 1 and 0, respectively, and gate input A is changed to 1 at $t = 40$ ns where it is then changed back to 0 at $t = 100$ ns. The gate output of G_1 changes exactly 20 ns after A changes, and finally the gate output of G_2 changes exactly 20 ns after G_1 changes.

 


Delays in Gates and Timing Diagrams

- The figure below depicts a timing diagram for a logic circuit with a delay element. Input X consists of two pulses: the first pulse is 2 microseconds wide and the second pulse is 3 microseconds wide. The delay element that tangents off of X has output Y, which is identical to the input, X, but it is delayed by 1 microsecond. What this means is that Y changes from a value of 1, 1 microsecond after the rising edge of the X pulse and then returns to a value of 0, 1 microsecond after the falling edge of the X pulse. Z, which is the output of this AND gate, should always be 1 during the time interval for which both X and Y have a value of 1. Assuming that there is a small propagation delay in the AND gate of ϵ .
- , then the output, Z, will provide the following timing diagram:

 


Delays in Gates and Timing Diagrams

 3. Obtain the timing diagrams for both gate outputs. Input waveforms are provided. All logic gates have the same propagation delay of 10 ns. Show glitches where applicable, identify glitch types.




Gates with More Inputs

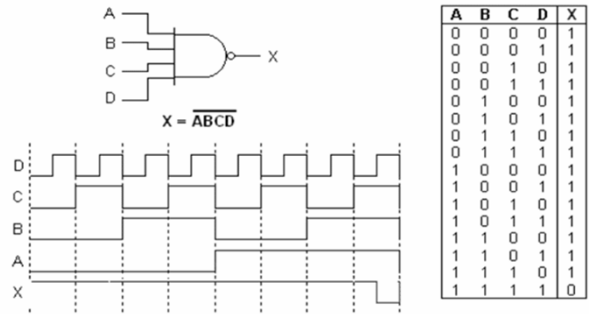- AND gate provides the AND operation of the digital signal




Gates with More Inputs

 - AND gate provides the AND operation of the digital signal




Gates with More Inputs

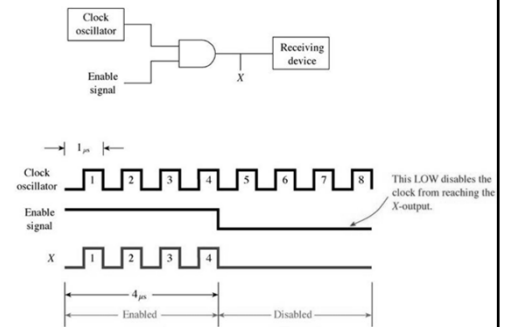- AND gate provides the AND operation of the digital signal





Electrical Equivalent: NOT Gate

 


Switch A - Open = "0", Lamp - ON = "1"
Switch A - Closed = "1", Lamp - OFF = "0"

Electrical Equivalent: AND Gate

 


 Electrical Equivalent: OR Gate**Electrical Equivalent: NOR Gate****Electrical Equivalent: Gate or Switch**


- A switch is a electrical/electronic component which make or break a circuit.

 **Electrical Equivalent: NOT Gate**


- A switch is a electrical/electronic component which make or break a circuit.

 **Electrical Equivalent: AND Gate**

- A switch is a electrical/electronic component which make or break a circuit.

  
**Electrical Equivalent: OR Gate**

- A switch is a electrical/electronic component which make or break a circuit.




Electrical Equivalent: NAND Gate

 - A switch is a electrical/electronic component which make or break a circuit.




Electrical Equivalent: NOR Gate

 - A switch is a electrical/electronic component which make or break a circuit.




Electrical Equivalent: XOR Gate

 - A switch is a electrical/electronic component which make or break a circuit.



Electrical Equivalent: XOR Gate

 - A switch is a electrical/electronic component which make or break a circuit.



Boolean Operations and Expressions

• Addition

$$\begin{aligned} 0 + 0 &= 0 \\ 0 + 1 &= 1 \\ 1 + 0 &= 1 \\ 1 + 1 &= 1 \end{aligned}$$



• Multiplication

$$\begin{aligned} 0 * 0 &= 0 \\ 0 * 1 &= 0 \\ 1 * 0 &= 0 \\ 1 * 1 &= 1 \end{aligned}$$




Laws of Boolean Algebra

- Commutative Laws
- Associative Laws
- Distributive Law

Commutative Law: Addition

- Commutative Law of Addition:


$$A + B = B + A$$

 

Commutative Law: Multiplication

- Commutative Law of Multiplication:


$$A * B = B * A$$

 

Associative Law: Addition

- Associative Law of Addition:


$$A + (B + C) = (A + B) + C$$

 

Associative Law: Multiplication

- Associative Law of Multiplication:


$$A * (B * C) = (A * B) * C$$

 

Distributive Law

- Distributive Law:

$$A(B + C) = AB + AC$$

 


Rules of Boolean Algebra

- | | |
|----------------------|-------------------------------|
| 1. $A + 0 = A$ | 7. $A \cdot A = A$ |
| 2. $A + 1 = 1$ | 8. $A \cdot \bar{A} = 0$ |
| 3. $A \cdot 0 = 0$ | 9. $\bar{\bar{A}} = A$ |
| 4. $A \cdot 1 = A$ | 10. $A + AB = A$ |
| 5. $A + A = A$ | 11. $A + \bar{A}B = A + B$ |
| 6. $A + \bar{A} = 1$ | 12. $(A + B)(A + C) = A + BC$ |

Rules of Boolean Algebra: Rule 1

• Rule 1

 


A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

OR Truth Table

Rules of Boolean Algebra: Rule 2

• Rule 2

 


A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

OR Truth Table

Rules of Boolean Algebra: Rule 3

Rules of Boolean Algebra

• Rule 3

 


A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

AND Truth Table

Rules of Boolean Algebra: Rule 4

Rules of Boolean Algebra

• Rule 4

 


A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

AND Truth Table

Rules of Boolean Algebra: Rule 5

Rules of Boolean Algebra

• Rule 5

 


A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

OR Truth Table

Rules of Boolean Algebra: Rule 6

Rules of Boolean Algebra

• Rule 6

 


A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

OR Truth Table

Rules of Boolean Algebra: Rule 7

Rules of Boolean Algebra

• Rule 7

 


A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

AND Truth Table

Rules of Boolean Algebra: Rule 8

Rules of Boolean Algebra

• Rule 8

 


A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

AND Truth Table

Rules of Boolean Algebra: Rule 9

Rules of Boolean Algebra


• Rule 9

 

Rules of Boolean Algebra: Rule 10

Rules of Boolean Algebra

• Rule 10: $A + AB = A$

 

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

AND Truth Table


A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

OR Truth Table

Rules of Boolean Algebra: Rule 11

Rules of Boolean Algebra

• Rule 11: $A + \bar{A}B = A + B$

 

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

AND Truth Table


A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

OR Truth Table

Rules of Boolean Algebra: Rule 12

Rules of Boolean Algebra

• Rule 12: $(A + B)(A + C) = A + BC$

 

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

AND Truth Table

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

OR Truth Table

DeMorgan's Theorem

- Theorem 1

$$\overline{XY} = \overline{X} + \overline{Y}$$

Remember:

- Theorem 2

$$\overline{X+Y} = \overline{X} \cdot \overline{Y}$$

BBCTS:

**“Break the bar,
change the sign”**

- Theorem 1: for n inputs

$$\overline{X_1 X_2 X_3 \dots X_{n-1} X_n} = \overline{X_1} + \overline{X_2} + \overline{X_3} + \dots + \overline{X_{n-1}} + \overline{X_n}$$


- Theorem 2: for n inputs

$$\overline{X_1 + X_2 + X_3 + \dots + X_{n-1} + X_n} = \overline{X_1} \cdot \overline{X_2} \cdot \overline{X_3} \cdot \dots \cdot \overline{X_{n-1}} \cdot \overline{X_n}$$

Universal Gate – NAND

□ **Universal Gate:** The GATES which can be used to develop other GATES

□ **NAND and NOR Gates**

 

□ We will learn

- NAND** gate can be used to replace an **AND** gate, **OR** gate, or an **INVERTER** gate.
- How a logic circuit implemented with **AND-OR-Invert (AOI)** logic gates can be re-implemented using only **NAND** gates.
- That using a single gate type, in this case **NAND**, will reduce the number of integrated circuits (IC) required to implement a logic circuit.



More ICs = More \$\$




Less ICs = Less \$\$

70


NOT Gate

symbol of NOT gate

 

where, $X = \text{NOT } A$

Double inversion

 


71

NAND Gate

AND Gate




AND GATE

 

AND gate NOT gate







$$X \text{ --- } Y \text{ --- } Z = \overline{X \cdot Y} = \overline{X} + \overline{Y}$$

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

 


X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

72

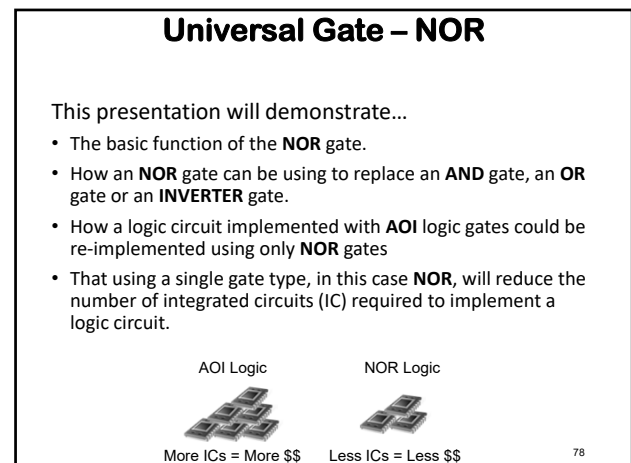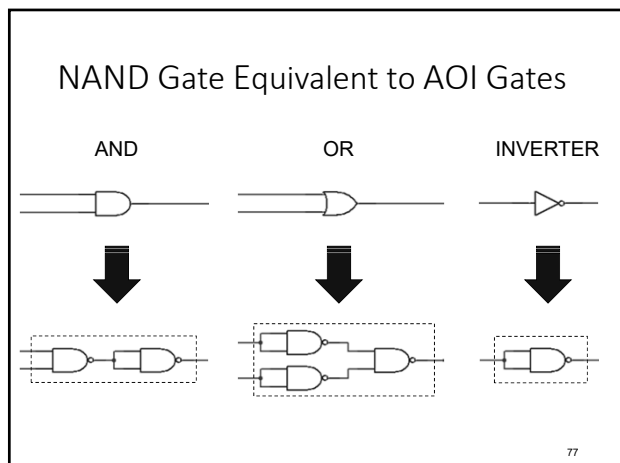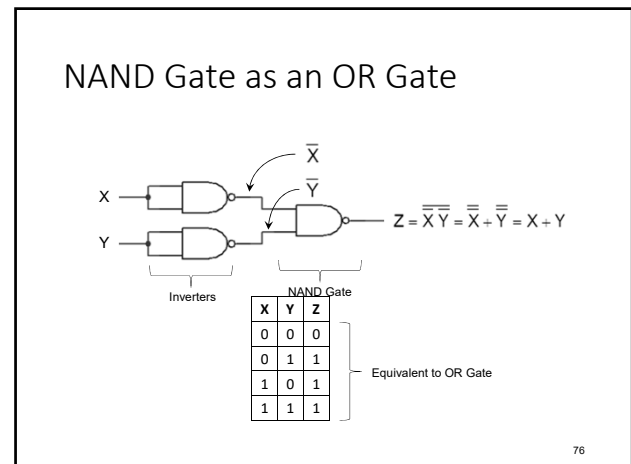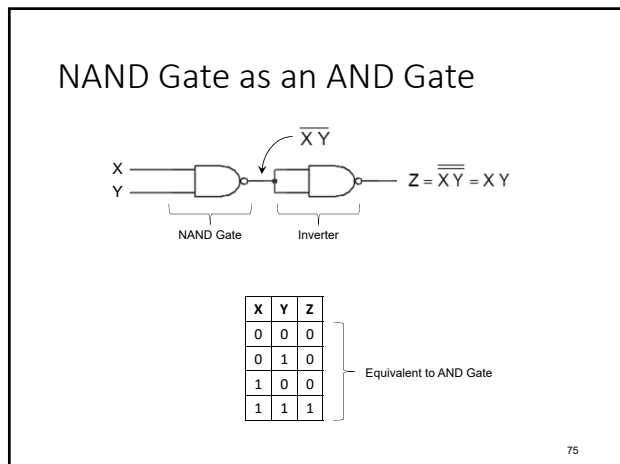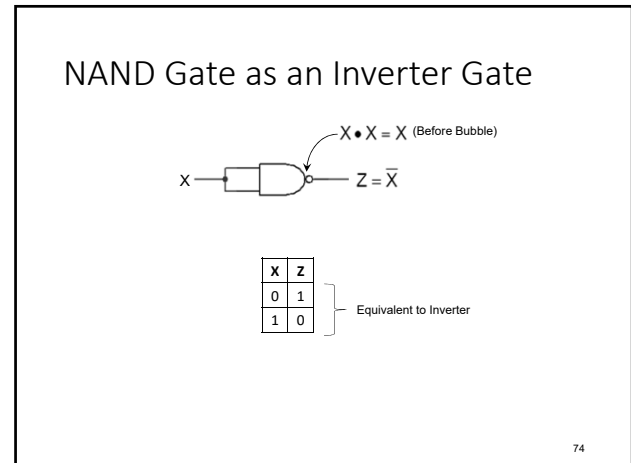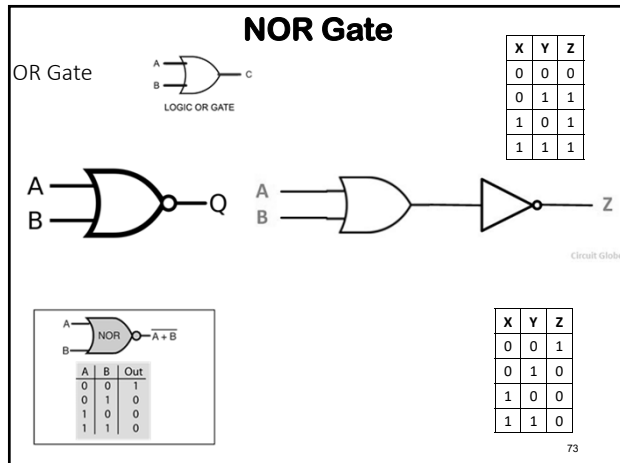


NOR Gate

 

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

79

NOR Gate as an Inverter Gate

 


X	Z
0	1
1	0

Equivalent to Inverter

80

NOR Gate as an OR Gate

 


X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

Equivalent to OR Gate

81

NOR Gate as an AND Gate

 


X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

Equivalent to AND Gate

82

NOR Gate Equivalent of AOI Gates

 


83

Logic Gates

Abc...

Universal Gates

 NAND gates are sometimes called **universal** gates because they can be used to produce the other basic Boolean functions.







84

Logic Gates

Abc...

Universal Gates

    NOR gates are also **universal** gates and can form all of the basic gates.




85


XOR Gate with NAND Gate



... is equivalent to ...

 

$$A \oplus B = A\bar{B} + \bar{A}B$$

 


$$X = A\bar{B} + \bar{A}B$$

$$X = A \oplus B$$

86

XOR Gate with NAND Gate

 


$$X = A \cdot \bar{B} + \bar{A} \cdot B$$

$$X = A \oplus B$$

87

XOR Gate: Boolean Expression

 

$$X = \overline{(A \cdot A \cdot B)} \cdot \overline{(A \cdot B \cdot B)}$$

$$X = \overline{(A \cdot A \cdot B)} \cdot \overline{(A \cdot B \cdot B)}$$

$$X = \overline{(A \cdot A \cdot B)} + \overline{(A \cdot B \cdot B)}$$

$$X = A \cdot \bar{A} \cdot \bar{B} + \bar{A} \cdot B \cdot B$$

$$X = A \cdot (\bar{A} + \bar{B}) + (\bar{A} + B) \cdot B$$

$$X = A \cdot (\bar{A} + \bar{B}) + (\bar{A} + B) \cdot B$$

$$X = A \cdot \bar{A} + A \cdot \bar{B} + \bar{A} \cdot B + B \cdot B$$

Now,

$$X = A \cdot \bar{A} + A \cdot \bar{B} + \bar{A} \cdot B + B \cdot B$$

$$X = 0 + A \cdot \bar{B} + \bar{A} \cdot B + 0$$


$$X = 0 + 0 + A \cdot \bar{B} + \bar{A} \cdot B$$

$$X = 0 + A \cdot \bar{B} + \bar{A} \cdot B$$

$$X = A \cdot \bar{B} + \bar{A} \cdot B$$

88

XNOR Gate with NAND Gate

 


$$X = A \cdot B + \bar{A} \cdot \bar{B}$$

$$X = \overline{A \oplus B}$$

$$X = A \odot B$$

89

XNOR Gate: Boolean Expression

 

$$X = \overline{(A \cdot A \cdot B)} \cdot \overline{(A \cdot B \cdot B)}$$

$$X = \overline{(A \cdot A \cdot B)} \cdot \overline{(A \cdot B \cdot B)}$$

$$X = \overline{(A \cdot A \cdot B)} \cdot \overline{(A \cdot B \cdot B)}$$

$$X = \overline{(A \cdot A \cdot B)} \cdot \overline{(A \cdot B \cdot B)}$$

$$X = \overline{(A \cdot A \cdot B)} \cdot \overline{(A \cdot B \cdot B)}$$

$$X = \overline{(A \cdot A \cdot B)} \cdot \overline{(A \cdot B \cdot B)}$$

$$X = \overline{(A \cdot A \cdot B)} \cdot \overline{(A \cdot B \cdot B)}$$

Now,

$$X = \bar{A} \cdot (\bar{A} \cdot B) + \bar{A} \cdot \bar{B} + (A \cdot B) \cdot (\bar{A} \cdot B) + (A \cdot B) \cdot \bar{B}$$

$$X = (\bar{A} \cdot A) \cdot B + \bar{A} \cdot \bar{B} + (A \cdot A) \cdot (\bar{B} \cdot B) + A \cdot (\bar{B} \cdot \bar{B})$$

$$X = 0 \cdot B + \bar{A} \cdot \bar{B} + (A) \cdot (\bar{B} \cdot B) + A \cdot 0$$


$$X = 0 + \bar{A} \cdot \bar{B} + A \cdot B + 0$$

$$X = 0 + \bar{A} \cdot \bar{B} + A \cdot B + 0$$

$$X = A \cdot B + \bar{A} \cdot \bar{B}$$

90

XOR Gate with NOR Gate

 

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	1
1	0	1
1	1	0

$$X = \bar{A} \cdot B + A \cdot \bar{B}$$

$$X = A \oplus B$$

91

Logic Gate Applications

LOGIC GATE APPLICATIONS

AND GATE APPLICATION :

In a simple application, an AND gate can be used to detect the existence of a specified number of conditions and, in response, to activate an appropriate action.


For example, an automobile's safety system requires that an audible signal must be produced to warn the driver when the seat belt is not engaged. The conditions for this are :

- i. That the ignition switch is on.
- ii. That the seat belt is unbuckled.
- iii. That the warning signal should last for a specified time and then turn off automatically.

The first two conditions can be represented by switches and the third by a timer circuit.

Fig.20 shows an AND gate whose high output activates a buzzer when these three conditions are met on its inputs.

Logic Gate Applications

 


- i. When the ignition switch is closed (i.e.ON) a HIGH is connected to the gate input A.
- ii. When the belt is not buckled, a HIGH is connected to the gate input B.
- iii. At the instant the ignition switch is closed, the timer is activated and produces a HIGH on gate input C.
- iv. The resulting HIGH gate output activates the alarm.
- v. After a specified time the output of timer circuit goes LOW. This disables the AND gate and turns off the alarm.

Logic Gate Applications


OR GATE APPLICATION :

 Let us assume that in a room with three doors an indicator lamp must be turned on, when any of the door is not closed.




The sensors are switches which are open when door is open.

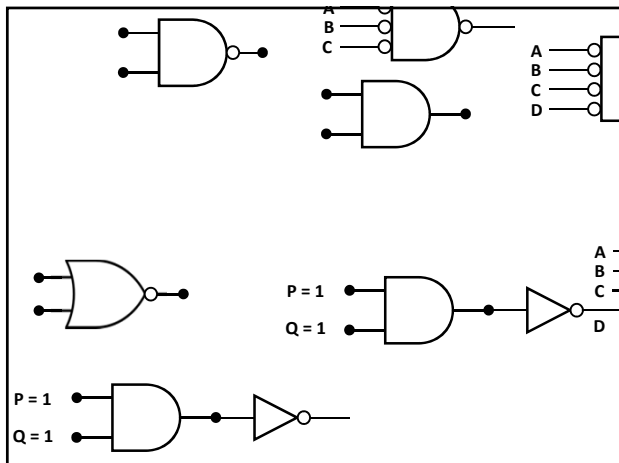This open switch creates HIGH level for the OR gate input as shown in Fig.21. If ANY or ALL of the doors are open, the gate output is HIGH. This HIGH level is then used to illuminate the indicator lamp.



Digital Circuit from Truth Table

 


Combinational Logic

Abc...

Combinational Logic Circuits

 In Sum-of-Products (SOP) form, basic combinational circuits can be directly implemented with AND-OR combinations if the necessary complement terms are available.




97

Logic Gates

Abc...

Combinational Logic Circuits

 An example of an SOP implementation is shown. The SOP expression is an AND-OR combination of the input variables and the appropriate complements.



98


Logic Gates

Abc...

Combinational Logic Circuits

When the output of a SOP form is inverted, the circuit is called an AND-OR-Invert circuit. The AOI configuration lends itself to product-of-sums (POS) implementation.

 An example of an AOI implementation is shown. The output expression can be changed to a POS expression by applying DeMorgan's theorem twice.



99

Logic Gates

Abc...

Exclusive-OR Logic


The truth table for an exclusive-OR gate is

Notice that the output is HIGH whenever A and B disagree.

The Boolean expression is $X = A\bar{B} + \bar{A}B$

Inputs		Output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	0


The circuit can be drawn as

 

Symbols:



Distinctive shape

 

Rectangular outline

100

Logic Gates

Abc...

Exclusive-NOR Logic


The truth table for an exclusive-NOR gate is

Notice that the output is HIGH whenever A and B agree.

The Boolean expression is $X = AB + \bar{A}\bar{B}$

Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

The circuit can be drawn as

 

Symbols:



Distinctive shape



Rectangular outline

101


Logic Gates

Abc...

Implementing Combinational Logic

Implementing a SOP expression is done by first forming the AND terms; then the terms are ORed together.

 Example Show the circuit that will implement the Boolean expression $X = ABC + ABD + BDE$. (Assume that the variables and their complements are available.)
Solution Start by forming the terms using three 3-input AND gates. Then combine the three terms using a 3-input OR gate.




102

Logic Gates

Abc...

Solution *continued...*

Circuit:

 

The result is shown as a sum of products.

It is a simple matter to implement this form using only NAND gates as shown in the text and following example.

103

Logic Gates

Abc...


NAND Logic

Example

Convert the circuit in the previous example to one that uses only NAND gates.

Solution

 Recall from Boolean algebra that double inversion cancels. By adding inverting bubbles to above circuit, it is easily converted to NAND gates:




104

Logic Gates

Abc...

NAND Logic

 Recall from DeMorgan's theorem that $AB = \overline{\overline{A}\overline{B}}$. By using equivalent symbols, it is simpler to read the logic of SOP forms. The earlier example shows the idea:



The logic is easy to read if you (mentally) cancel the two connected bubbles on a line.


105

Logic Gates

Abc...

NOR Logic

 Alternatively, DeMorgan's theorem can be written as $A + B = \overline{\overline{A}\overline{B}}$. By using equivalent symbols, it is simpler to read the logic of POS forms. For example,



Again, the logic is easy to read if you cancel the two connected bubbles on a line.


106

Logic Gates

Abc...

Pulsed Waveforms

 For combinational circuits with pulsed inputs, the output can be predicted by developing intermediate outputs and combining the result. For example, the circuit shown can be analyzed at the outputs of the OR gates:




107

Logic Gates

Abc...

Pulsed Waveforms

 Alternatively, you can develop the truth table for the circuit and enter 0's and 1's on the waveforms. Then read the output from the table.




Inputs				Output
A	B	C	D	X
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	1	1

108

Truth Table from Digital Circuit

 - Write down the truth table indicating intermediate variables




A	B	A+B	A.B	$(A+B).(\overline{A.B})$
0	0	0	1	0
0	1	1	1	1
1	0	1	1	1
1	1	1	0	0

?

Truth Table from Digital Circuit

 - Write down the truth table indicating intermediate variables



A	B	A.B	A.B	A+B	$(A.B).(A+B)$	$(A.B).(A+B)$
0	0	0	1	0	0	0
0	1	0	1	1	1	1
1	0	0	1	1	1	1
1	1	1	0	1	0	0

?

Truth Table from Digital Circuit

